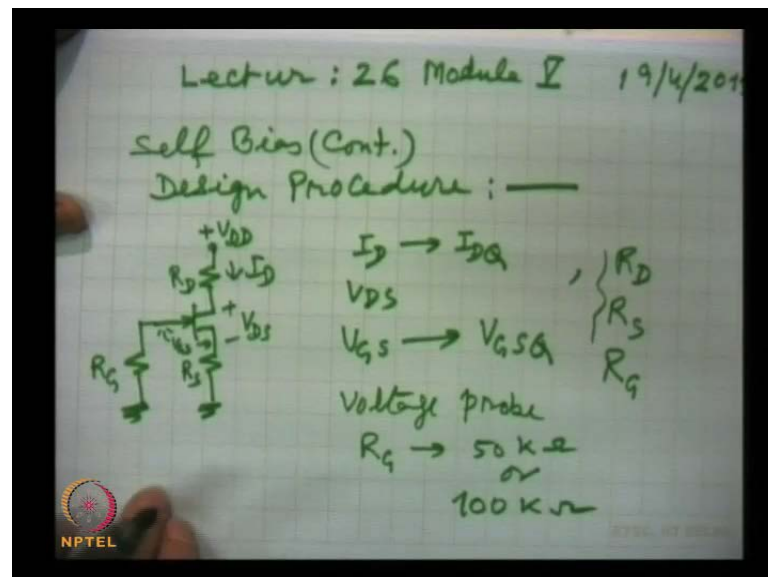


FETS and MOSFETS
Prof D.C.Dube
Department of Physics
Indian Institute of Technology, Delhi

Module No. # 05
Lecture No. # 05
Self Bias (Contd.) Design Procedure

(Refer Slide Time: 00:28)



We continue our discussion, on self bias. Now, we take some design procedure that is how to know the components the values of various a resistances and voltages and current in the self bias circuit this comes under design procedure. So, let us consider first the circuit the simple circuit which we were discussing was this


(No audio from 00:59 to 01:31)

This was the self bias circuit and design implies that we should know the value of current I_D at the Q point. So, this actually we write as I_{DQ} at and the voltage V_{DS} and this a gate source voltage V_{GS} and at the Q point this is also to be noted and this we shall write V_{GSQ} , Q point the quotient point or operating point. We have to decide and a since mostly these procedures which we are doing they are going to be adapted to make a

amplifying circuit out of a MOSFET or junction field effect transistor. So, from the characteristics, how we arrive at these values that we will see. And then we require the value of this resistance R_D R_S about R_G we have already talked R_G is a there is no current flows through this resistance.

So, actually, R_G this probe this is a gate terminal acts as a voltage probe a voltage probe has to have a very high resistance. So, normally, R_G is taken 50 kilo ohms or 100 kilo ohms. So, this we say now this is known the these two resistances have to be determined for the circuit and that will be governed by the drain characteristics what are what type of drain characteristics drain characteristic tell us the amount of drain currents which flow in the circuit and what are the various voltages. So, this all comes under design procedure and we proceed to find out these values.

(Refer Slide Time: 04:24)

 

Now, the two equations we arrived earlier, by simple summing up of voltages these equations where V_{DD} equal to V_{DS} plus $I_D R_D$ plus R_S this was 1 equation, which comes simply when we sum up voltages in the output circuit. Another equation is obtained when we sum up voltages here and from there came the equation V_{GS} equal to minus $I_D R_S$ this can be return in the form I_D the drain current is equal to minus V_{GS} by R_S this is the equation of a straight line. And when this a straight line is plotted on the trans conductance curves of the device. That is this is trans conductance curve and


this is the line when to be plot on this is like that this is called bias line and the slope it is slope of bias line gives the this depends on the value of R_s .

So, if we choose R_s that will shift this slope; that means, thus base line will move across this point. So, once we choose the operating point Q than we know the slope and thus R_s is known. And from these curves we also know the value of the drain current at Q point and V_{GS} at Q point. So, three parameters are known R_s the resistance in the circuit is known that will be determined by the slope and slope is dependent on where we choose the operating point. So, normally we choose somewhere, in the center enhance the slope will give the value of R_s and this slope of the line is actually minus 1 by r.

So, this will give the value of R_s . And at the operating point what is this drain current and what is this voltage? Now, few points we discussed, when we were discussing, the bipolar transistor and it is circuit. Than, we will recall from there that these are the DC values and normally in an amplifier we will use AC signals. So, the variation of current will occur taking this DC value at it is a center. So, the variations will be this is the DC value than AC variations will be along this. And similarly, the input voltage is the gate source voltage.

So, when superimpose AC signal on this than these variations will occur a across this Q point value of the gate source voltage. So, this way three parameters are now known the I_{DQ} , V_{GSQ} and resistance R_s all are known than the this V_{GS} and this I_D this will give you actually, the value of a V_{DS} at the Q point also let us, see the output characteristics the drain characteristics they, where like this.

(Refer Slide Time: 09:14)

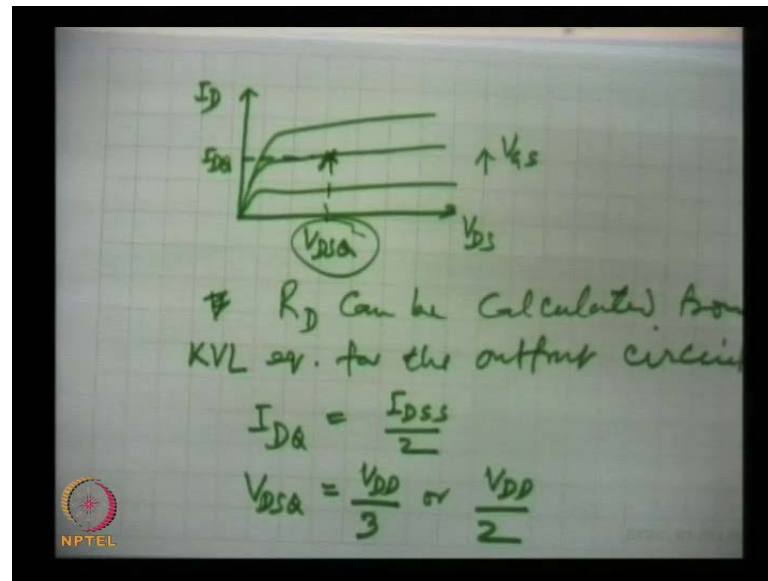


This is V_{GS} V_{DS} I_D and if we choose the operating point say for example, here than this is I_{DQ} the same as we have we got I_{DQ} here. So, that we mark here and from we extended and we get V_{GSQ} I_{DQ} and this is V_{DSQ} . So, once V_{DSQ} is known the battery, which we use in the circuit this, which is the single DC source in the circuit normally for the devices. This is the currently used integrated circuits make use of V_{DD} of 5 volts, when discrete devices are use than this voltage can be a high can be 10 or 12 15 30.

So, this way V_{DD} is known and then we use this first equation which we have we had written this one this equation here now I_{DQ} is known R_S is known so this is known, this is known and V_{DSQ} is known V_{DD} that is the battery source, which we are using that we a anyway no. So, this way R_D can be calculated. So, this way we find out all the parameters of the circuit the R_D can be calculated from Kirchhoff's voltage law equation for the output circuit. Now, I_{DQ} and V_{DSQ} this is I_{DQ} this is V_{DSQ} they are taken here from the these, a drain characteristics there is another procedure, which is a often employed and that is it is the thumb rule that I_{DQ} can be safely taken as I_{DSS} by 2.

So, wherever, the largest current a through the device this parameter is normally, given by the manufacturer. So, once it is known, when it is safest to take I_{DQ} as half of I_{DSS} similarly, V_{DSQ} can be taken as one third of V_{DD} or even half of this. So, this way

instead of a using these characteristics $I_D Q$ and $V_{DS} Q$ can be known from here. So, we have determined all the parameters of this circuit $R_D R_S V_{DS} I_D V_{DD}$ and R_G and that is the completed design of the self bias circuit. Self bias is often used for a junction field effect transistor and it can also be used, where negative V_{GS} is required in the p MOSFETS particularly.

(Refer Slide Time: 13:37)

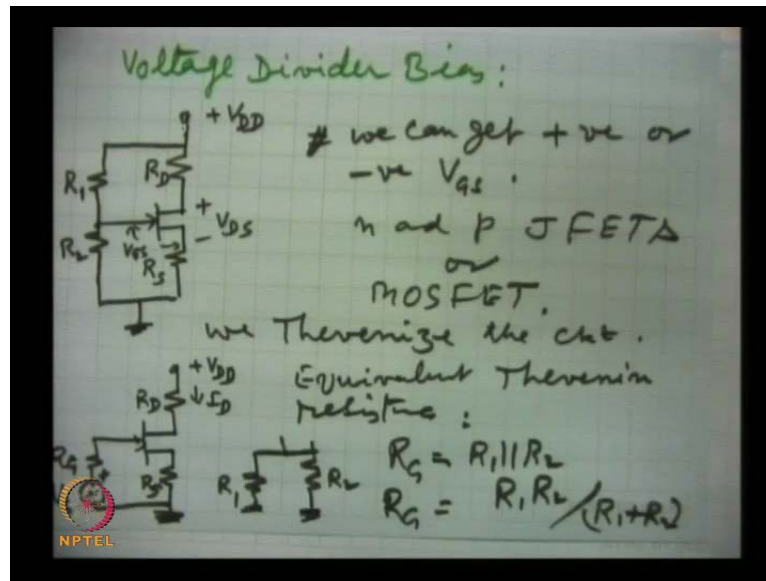


Now, the another biasing circuit is voltage divider bias it say broader circuit and infect it can be used for getting positive or negative gate source voltage both can be by adjusting proper resistances this can be use. So, this is having a wider use and of course, for e MOSFET this is the one, which is used. Now, the circuit is this is a V_{DD} this is $R_D R_S R_1$ and R_2 here this voltage V_{DD} is divided this network $R_1 R_2$ this x as a voltage divider. So, that is why the name voltage divider here this is V_{DS} and this is V_{GS} and this can be used, because we can get this an important. We can get positive or negative V_{GS} therefore, it can be used for n and p JFET'S or MOSFET'S any kind of MOSFET, this circuit first we Thevenize it and the Thevenized by applying.

Thevenize theorem we Thevenize the circuit and what we get is this the Thevenized circuit is this. This V_{DD} and this is the resistance we will equivalent the Thevenize equivalent of this two resistances we will tell that how this is determined and this is the voltage source V_G this is $I_D R_D$ and this is R_S . This is Thevenize equivalent circuit and here the value of a equivalent thevenize resistance. Just you remind you that by

applying Thevenize theorem we can find out this resistance than this resist for this resistance this D C source is to be grounded now, what is the equivalent resistance between these points between this and ground.

So, that is to be determined now once we ground this terminal also this terminal also than this is like this. This is R 1 this is R two so, as for as this point is concerned this Thevenize resistance are this is equal to the parallel combination of this two resistances, which is R G is simply, $R_1 R_2$ by $R_1 + R_2$ this is thevenize equivalent resistance. The voltage is what is the voltage? Which this, V_{DD} produces between gate and source.


(Refer Slide Time: 18:51)

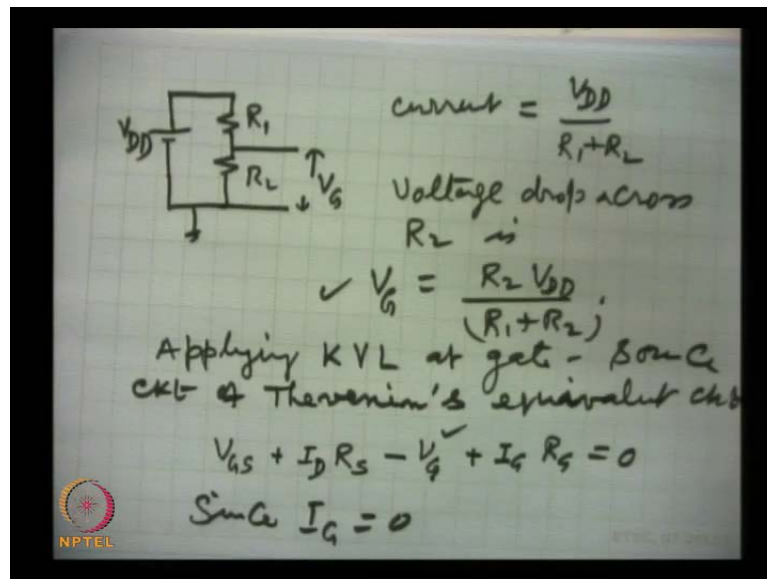

So, the equivalent circuit actually, will be this, this is V_{DD} and this is the two resistances this is R_1 this is R_2 and here we have to find out this is V_G . So, obviously, the DC current through this circuit is the current is V_{DD} by $R_1 + R_2$. And the voltage drop across R_2 is simply, that is V_G is simply $R_2 V_{DD}$ this current into this resistance so R_2 into this current so $R_1 + R_2$ this is V_G . Now, once this is a there this current we take as I_G and we apply the summation of voltages that is Kirchhoff's voltage law in the gate source circuit of this. So, applying Kirchhoff's voltage law at gate source circuit of Thevenize's equivalent circuit we get the equation V_{GS} plus $I_D R_S$ minus V_G plus $I_G R_G$ is equal to 0, here this is $V_G S$.

So, we start with we are finding out the summation of voltages we are writing the equation for summation of voltages in this circuit. So, V_{GS} than I_D into R_S than minus V_G plus I_G and R_G equal to 0 where this V_G is given by this expression and a I_G here is a 0. Since, why I_G is zero? Because all gates are operated in reverse bias, so, I_G is 0 and then we get from here when we put.

(Refer Slide Time: 22:27)

 

So, this term goes and we simply get V_{GS} is equal to V_G minus $I_D R_S$ this is the fundamental equation. And this clearly shows, that V_{GS} the gate source voltage can be obtained either negative or positive, if it is to be positive than V_G must be greater than $I_D R_S$ the drop across this resistance should be smaller than V_G that will give positive value of V_{GS} . Or if negative value is decide than the drop across resistance R_S has to be higher than V_G . So, this is actually, this is the equation of load line or call it bias line and this is to be plotted on the transfer characteristics of the device to find various important parameters. So, when we plot these here these are the characteristic this is V_{GS} I_D the output current and input voltage gate source voltage.

And this is the equation of a straight line from here at this point V_{GS} is 0, when V_{GS} is zero than current I_D from here we will get I_D equal to V_G by R_S this is the point and to get this point here I_D is 0. So, this is the point, which gives the value of V_G and where this a load line crosses cuts the transfer characteristics this is the Q point. And a now we will proceed to find out for example, what is how to get negative and positive

voltages first let us take for N MOS on N MOSFET where, V G S is positive and for positive from this equation base line equation load line equation V G has to be greater than I D R S. We substitute here the value of a V G value of V G is here in this equation. So, this we substitute here and let us, see what we get.

(Refer Slide Time: 26:36)

$$\frac{R_2 V_{DD}}{(R_1 + R_2)} > I_D R_S$$


$$\text{or } \frac{V_{DD}}{(1 + R_1/R_2)} > I_D R_S$$

if R_2 is chosen very large,
 $R_2 \rightarrow \infty$

So, when we substitute the value we get $R_2 V_{DD}$ by $R_1 + R_2$ this should be this should be greater than $I_D R_S$ or V_{DD} by $1 + R_1/R_2$ should be greater than $I_D R_S$. This in equality can be satisfied; obviously, if R_S is chosen very large, if $R_S R_2$ is chosen very large than this in equality can be easily satisfied in the limiting case R_2 in this circuit in the voltage divider circuit R_2 can be taken as infinity. Almost approaching infinity and in fact it can be taken as infinity a approaching R infinity in what is R infinity, the absence of the resistance. If R_2 is removed from the circuit, than we satisfy this in equality easily.

So, the circuit is reduce to this we remove from here R_2 . So, that the circuit is this is N M O S this is R_S and this is R_1 this is V_{DD} and this is R_D . Here we will absorb V_G this is the circuit biasing circuit just one resistance here instead of in the self bias the resistance was here. So, we can bias we can get a positive gate source voltage, which is required for example, for N M O S here this is N M O S and if we intent to get a negative voltage.


(Refer Slide Time: 30:14)

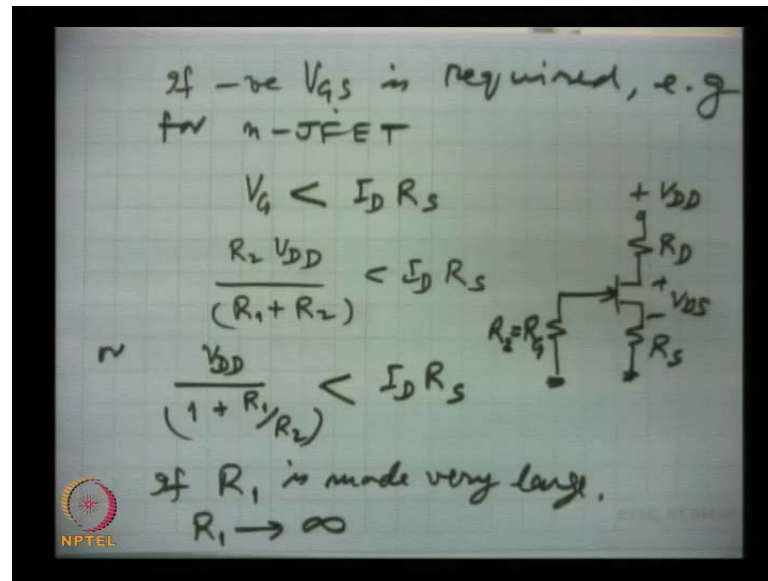

When negative gate source voltage is required negative V_{GS} is required for example, for biasing n JFET or p MOS then, V_G has to be smaller than $I_D R_S$ and when we substitute for V_G . We get is less than $I_D R_S$ or $V_{DD} \frac{R_2}{R_1 + R_2}$ this is this has to be less than $I_D R_S$ this equality in equality can be satisfied, if R_1 is very large, if R_1 is made very large and in the limiting case R_1 can be infinitely high. That means, if we remove R_1 than we will get a negative gate source voltage and the circuit will be the same as we have got for self bias that is the this circuit will be reduced voltage divider bias, if we remove this resistance R_1 here to make it infinity that will reduce this circuit to this form.

We are this is V_{DD} , R_D , R_S and this voltage this is of course, V_{DS} this is V_{GS} and this is R_2 , which is same as we have taken earlier R_J . So, this is the circuit to get a negative gate source voltage from the voltage divider bias and we can get the positive also as we have seen in the previous case. So, this way this voltage divider bias can be used and this is the one, which is a quit widely used with the most devices and a thus we finish the biasing of the FETS and MOSFETS any kind of FET junction field effect transistor or MOSFET can be biased in by using these two biasing networks.

(Refer Slide Time: 34:04)

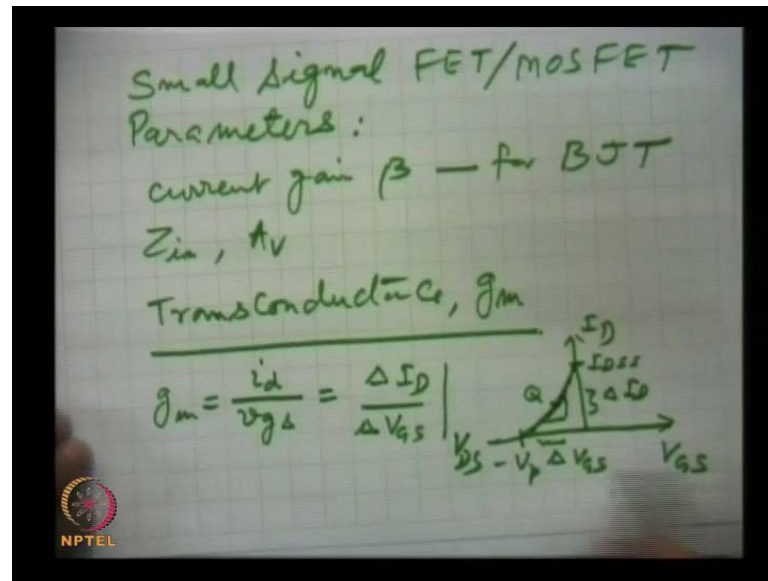

The next thing, which we are going to have that is a small signal of parameters, a small signal F E T or MOSFET parameters this we are going to a study now for V J T. We have seen that a beta the current gain beta for bipolar junction transistor B J T was most popular and this was the ratio of output current to input current. This parameter beta appear in the expressions for input impedance z_{in} or voltage gain and. So, on field effect transistor or MOSFETS they are voltage operative device here the important parameter is Trans conductance of the device, which is written as G M.

So, G M Trans conductance parameter is a most important parameter for a junction field effect transistor or for MOSFET. And first we will define it and then we will go for other is no signal parameter. So, Trans conductance G M this is defined as, because we will be concerned with the ac operation of the device. So, we can define the AC drain current by a c. So, when on the Q point when we superimpose the signal what is I D and V G S the ratio of the two, which can be shown equal to let us, see for first for A F E T the J F E T here this is the Trans conductance curve and a this is a V p and this is I D this is V G S.

So, this curve is the Trans conductance curve and at the operating point, we draw a small tangent and we find out, this is change in the drain current I D and this is the change in a gate voltage. So, this ratio can be return as change in ID by change in V G S at constant V D S this is the way it is defined. Now, this is obvious that, if we choose Q point here here here here than every where G M is changing and G M is highest near this I D D S

show circuit drain source current when gate is shorted to source. This is the highest value and the slope is highest here. So, here this G M will have highest value the highest value of G M is designated as a g_{m0} this is the highest value of G M.

(Refer Slide Time: 38:46)

$g_{m0} \rightarrow$ highest value of g_m
 which is g_m near I_{DSS} point
 g_{m0} can also be obtained from


$$g_{m0} = \frac{2 I_{DSS}}{|V_p|}$$

$$g_m = g_{m0} \left(1 - \frac{|V_{gs}|}{|V_p|} \right)$$

Which, is actually, which is the Trans conductance value near I_{DSS} point on the trans conductance curve. Now, g_{m0} can be determine as we are seeing from the trans conductance curve here by taking this operating point in the vicinity of I_{DSS} or it is g_{m0} can also be obtained from the simple relation g_{m0} is equal to $2 I_{DSS}$ by V_p from here also g_{m0} can be obtained. Now, once g_{m0} is known either from that graph directly or by using these two parameters. Then we require Trans conductance value at the operating point and as I said because the slope is changing. So, G M is changing quite a bit along the Trans conductance curve.


So, for accurate analysis at the Q point the value of G M the Trans conductance is required and. So, from g_{m0} the maximum value, which is either, provided by the manufacturer or can be obtained from the data provided by the manufacturer. We can find g_m for any value of V_{GS} depending on our Q point. We can get from here this is the equation, which can be used to get value of trans conductance parameter from g_{m0} by substituting the value of at what gate source voltage we require this value. We can get from here where here this is the pinch of voltage.

(Refer Slide Time: 41:49)

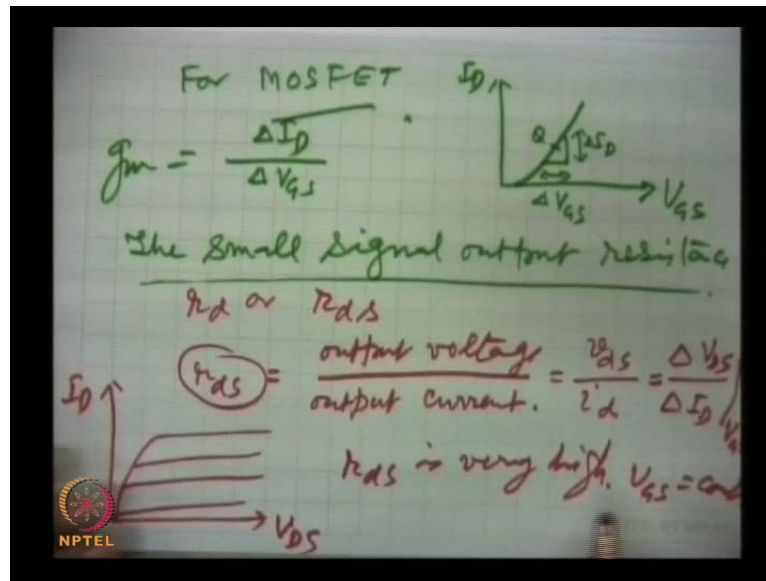


This example we took for is graph we took for a J F E T for M O S F E T the curve will be like this and here we choose the operating point and we draw. So, the same thing we get the value of I D change in I D and this is the change in V G S the ratio will give g m for M O S F E T at the Q point. The another a small signal parameter, which we require and that is the small signal output resistance this is a defined, as it is return as either R D or as R D S. This is actually, the resistance of the channel in the circuit and this is defined, R D S is equal to output voltage by output current that is V D S AC value of the drain source voltage and the AC drain current, which is same as changes in V D S by changes in the drain current at this is constant V G S constant. This is actually, if we look at the drain characteristics this was I D and this is V D S than this resistance represents this slope of the drain characteristics in the saturation region.

(Refer Slide Time: 45:03)

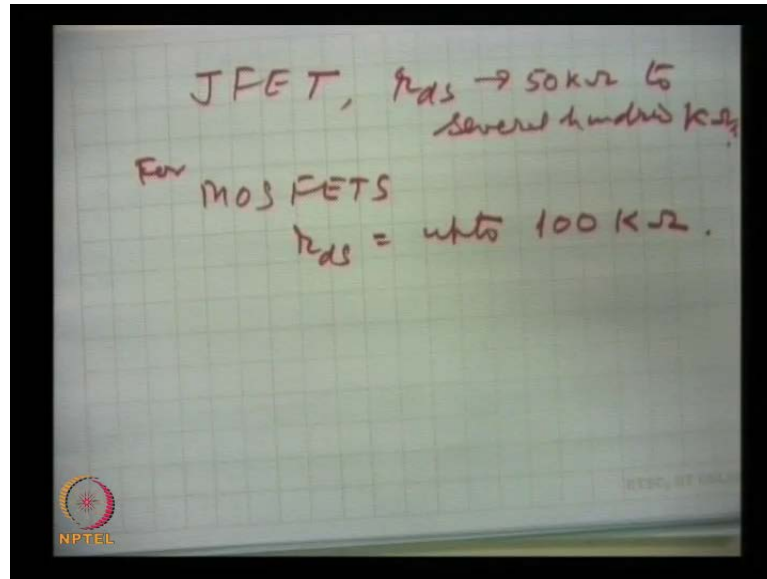

Which is a nearly, horizontal and that state that r_{ds} is very large very high and for J F E T, R_{DS} or simply R_D this is 50 kilo ohms to several hundred kilo ohms and for M O S F E T r_{ds} is up to 100 kilo ohm. Actually, when we take the circuit actual analysis we will see that normally, a smaller resistance will be put in parallel with this r_{ds} . So, r_{ds} effect that way will be negligibly a small. So, this two most important parameters we discussed, one was trans conductance, which will appear for example, we want to know what is the voltage gain of a M O S F E T amplifier than their essentially one of the parameters, which will appear is a trans conductance parameter. And then we discussed, about the a small signal output resistance of the device and that is normally, very high for J F E T or for M O S F E T the next thing, which we take that is a small signal F E T model.

(Refer Slide Time: 47:06)

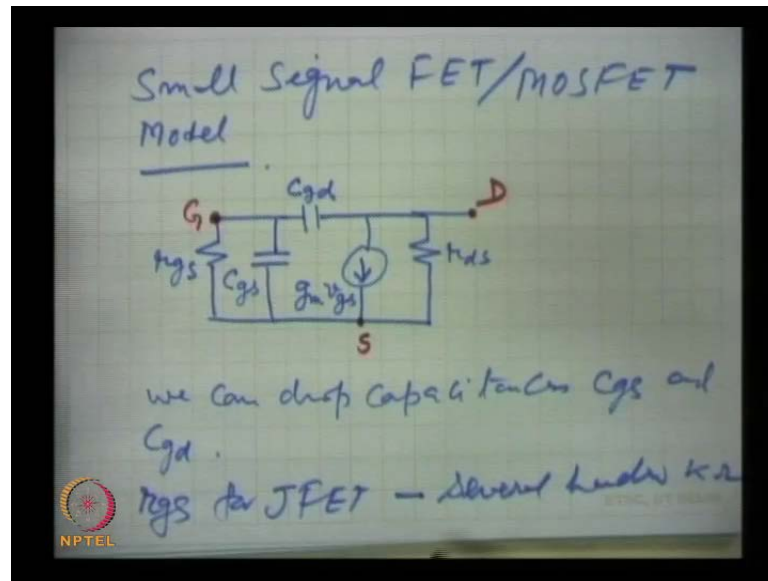

A small signal F E T and also the same model for M O S F E T, when we were discussing, the bipolar transistor and it is a model we have already seen the utility. In a circuit, when the device is replaced by it is modal that enables the analysis by using simple algebraic equation summation of voltages etcetera or current. We can find the value of output voltage versus input voltage, which will be the voltage gain similarly, if input impedance is to be determined or any other parameter is to be determined than a small signal modal is very useful.

So, we are now developing a small signal modal for F E T, which also applicable for M O S F E T S. Now, any two conductors when separated with a dielectric insulator there is a capacitance associated. So, when we talk of the exact modal of the device there are several conducting paths in the device there will be capacitances. For example, between gate and source there will be a capacitance similarly, between gate and drain there will be a capacitance. So, if we talk of the exact module, which we will simplify of course, we will have to take into a account these capacitance and all kinds of resistance. So, the modal for the device will be this.


(No audio from 49:36 to 50:07)

This is the gate terminal gate terminal here and this is this whole is source and here is drain this is that a output is resistance. Which we talked R D S and this is the current source and this is $g_m v_{gs}$ and this is the capacitance between gate and drain and

this is the capacitance between gate and source and this is the resistance between gate and source. This is the exact modal, but we can simplify for example, we are taking of moderate frequencies and this frequencies will be normally up to few tense of kilo Hertz. They are these impendence offered by this two capacitances they are very high and very high impendence's becomes almost they can be taken out from the circuit.

So, we can drop capacitances C_{gs} and C_{gd} this capacitance's we can drop for the frequencies, which are currently presently under discussion. Also this resistance between gate and source is very high for j f e t this is hundreds of kilo ohms r_{gs} for J F E T. This is several 100 kilo ohms and for M O S F E T S for M O S F E T S at least two orders of magnitude higher.

(Refer Slide Time: 53:22)

 

So, this resistance can be also taken out than what we are left is this modal, this is gate terminal, this is source, and this is drain and this is R_{DS} and this is the current source. This has the dimensions of the current source, because g_m we know g_m is I_D versus v_{gs} . So, g_m into v_{gs} is equal to I_D . So, this is the current source and here and this current source is that the magnitude of this current is dependent on the gate source voltage whatever, voltage we apply here v_{gs} . So, this is the modal, which we will be using and remember it is very simple modal this is one resistance, which we will see when we put actual resistance here, than the two resistances in parallel one very high

resistance one low resistance than the effective resistance of the parallel combination will be closer to the a smaller resistance.

So, this will also disappear and so the current source remains and this we are going to use for the analysis of F E T amplifiers. We are going to a study three amplifiers the common source amplifier, the common drain amplifier and common gate amplifier like B J T can be used in three different configurations. So, is the case, with F E T this can also we used for three different configurations. So, we will drive the useful parameters for all these amplifiers using this modal. And we will see that we will come to a net conclusion that like common emitter amplifier in B J T common source amplifier with MOSFETS and a with the FET'S is most widely used and we will be is studying that.