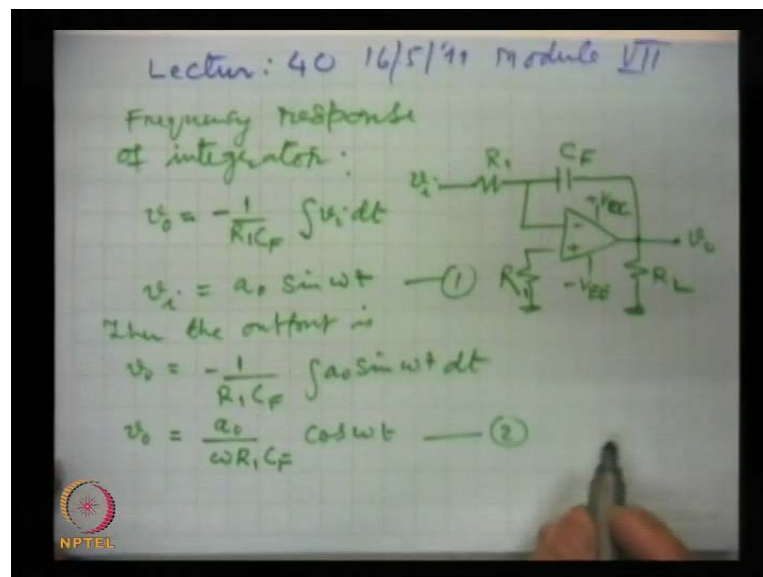


Electronics
Prof. D.C. Dube
Department of Physics
Indian Institute of Technology, Delhi

Module No. # 07
Differential & Operational Amplifiers
Lecture No. # 40
Frequency Response of Integrator

We were discussing the Frequency Response of an Integrator.

(Refer Slide Time: 00:34)




The basic integrating circuit, integrating amplifier using operation amplifier, we have already discussed and it was this, (No audio from 00:44 to 01:04) this is the input signal v_i and resistance R_1 , capacitor C_F and of course, these power supply is there. This is load resistor across which, we take the output, and this is to reduce the offset effects, about offset effects we will definitely talk. So, this is around R_1 and we have seen that the output of this is minus 1 by $R_1 C_F$ integration $v_i dt$, where v_i is the input signal.

And if we take that input signal v_i is expressed as, $a_0 \sin \omega t$, then the output is then the output of the integrator is v_o minus 1 by $R_1 C_F$ and integration $a_0 \sin \omega t$

d t, and this gives v 0 equal to a 0 omega R 1 C F cos omega t. This is we take as first and this is the second (Refer Slide Time: 02:56).

(Refer Slide Time: 03:06)

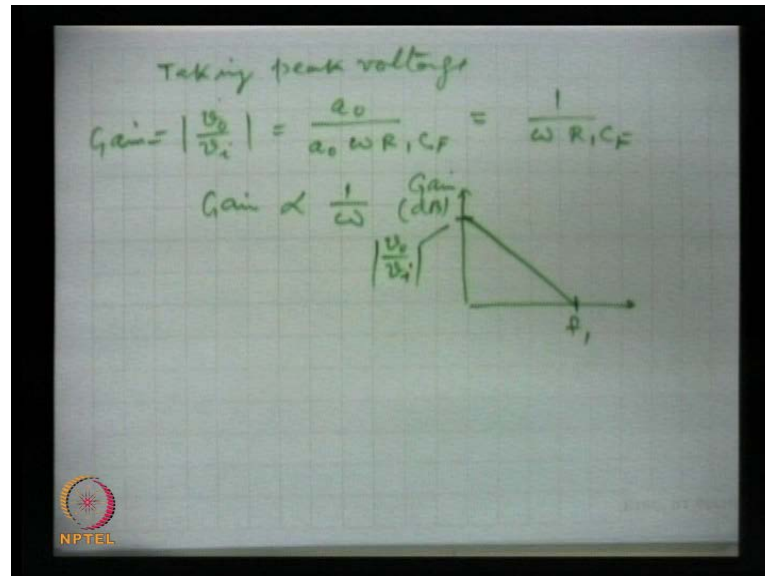


Then we can write the ratio of the two for the peak voltages, taking peak voltages both at the input and output, the ratio which is gain v 0 by v i its magnitude is, a 0 by a 0 omega R 1 C F and so, it is equal to 1 by omega R 1 C F and this is gain, gain of the integrator.

So, what we are seeing that, the gain is frequency dependent. As the frequency is, this angular frequency is omega, which is 2 pi F. So, as the frequency F increases, the gain falls. So, gain is proportional **proportional** to 1 by omega, the frequency and the plot for this is, this is the frequency f 1 (Refer Slide Time: 04:26), at which the gain falls to 0, this is gain in d B, and this value this represents v 0 by v i this magnitude of this quantity.

Now, the gain is falling and it can be shown that, this fall is minus 20 d B per decade change in frequency. So, if frequency becomes 10 times, then gain becomes one-tenth that is the meaning and the gain falls. And here, the f 1 this frequency, this is frequency f 1 is given by 1 by 2 pi R 1 C F, this we can get from here actually, this is gain and when at the frequency at which gain falls to 0 is given by this (Refer Slide Time: 05:41). And so, this is **this is** the frequency response of the basic integrator, this integrator circuit.

And now we have discussed that, there is a problem with this circuit. And the problem arises, because of the offset, offset currents and voltages and the capacitor, gets charged and it is amplified and there is a output, even when there is no input; and these problems can be tackled by attaching a resistor along with the capacitors in shunt.

(Refer Slide Time: 06:45)

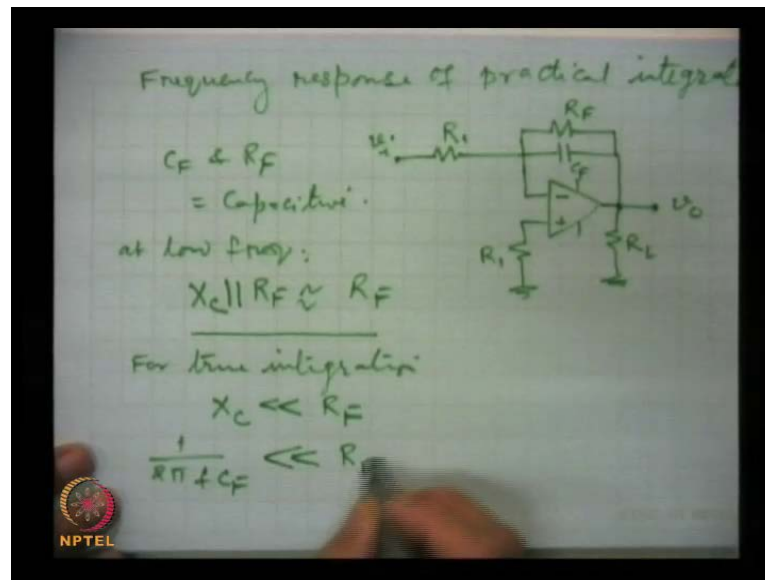

So now, we discussed the frequency response of a practical integrator, frequency response of practical integrator. So, the circuit which we are considering is now this (Refer Slide Time: 07:02), (No audio from 07:03 to 07:31) this is R_F the resistance we have included; and this is C_F and this is connected here and this is load across, which we take the output and here, we connect the input. So, this is the practical integrator.

Now, remember the basic that, true integration occurs when the **when the** impedance of this combination of C_F and R_F is capacitive, and this will be capacitive only when, this the effect of this capacitance dominates (Refer Slide Time: 08:29). So, and we know that at low frequencies, **at low frequencies** the parallel combination of the reactance of this capacitance in parallel with R_F at low frequency, this will be very high **impedance** reactive impedance of the capacitance will be very high, and this parallel combination will give the effective value as R_F .

So, that means at low frequency is this, inclusion of this resistance R_F , this limits the lower frequency for integration; that means, at very low frequencies we had this condition is satisfied, the output will not be the true integration of the **of the** input. And


then, so for true integration, for true integration this reactance should be very small as compared to R_F ; that means, $\frac{1}{2\pi f C F}$, this should be very small as compared to R_F .

(Refer Slide Time: 10:30)

we define a critical freq. f_c ,
 $X_c = R_F$
 $\frac{1}{2\pi f_c C F} = R_F$
 $f_c = \frac{1}{2\pi R_F C F}$
 f_c gives break frequency in the response.

And we can define a critical frequency beyond which, integration will be alright. So, we define a critical frequency, f_c we define a critical frequency f_c such that, X_c is equal to R_F . And substituting the value of this, $\frac{1}{2\pi f_c C F}$ now into $C F$, this is equal to R_F or the frequency f_c is equal to, from here $\frac{1}{2\pi R_F C F}$, this is the critical frequency. And this will give; f_c give a break frequency gives break frequency in the response in the response.

(Refer Slide Time: 11:40)

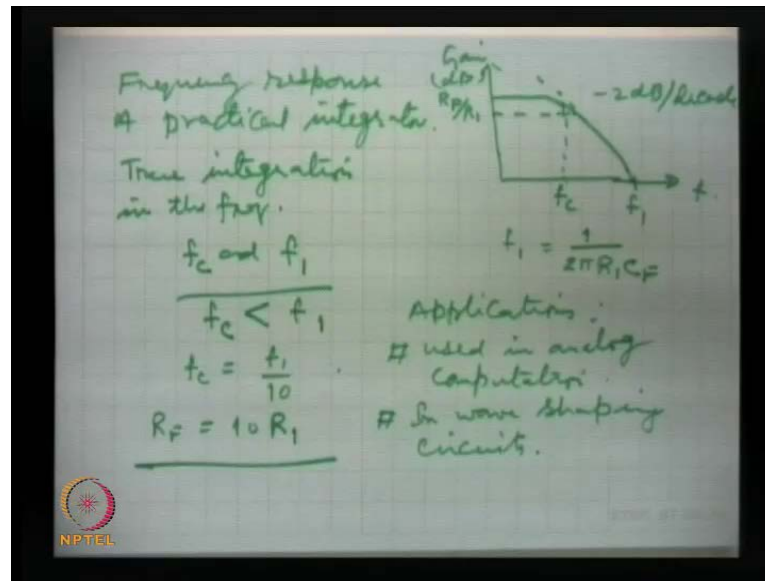

And the response is this, (No audio from 11:42 to 11:53) this is frequency, this frequency is f_1 and this is at, this is the 20 dB (()) and here (Refer Slide Time: 12:16), this is the 3 dB line and this gives, f_c this cut of frequency which we have written this f_c , this is this value and for this f_1 we have written earlier, f_1 is equal to where gain falls to 0 dB, this is gain in dB and this is R_F by R_1 gain. So, and this gain is this frequency is $\frac{1}{2\pi R_1 C_F}$.


There is a difference in two break frequencies, f_1 this is because this resistance will be smaller than the resistance, which is used with the capacitor. So, this contains the first resistance here, this is R_F and R_F is definitely higher at least 10 times, normally 10 times of this (Refer Slide Time: 13:33). So, this is the frequency response of **this is the frequency response of** practical integrator.

And what we see, that below f_c frequency which we can calculate from this expression, below f_c true integration will not occur. So, true integration **true integration** in the frequency limit, in the frequency between the frequency f_c and f_1 . So, actually f_1 is chosen quite high as compared to f_c ; f_c we choose very high as compared to f_1 and **in** it is a thumb rule that, f_c is one-tenth of f_1 , and **and** in that case R_F will be ten times of R_1 .

This resistance is ten times of this resistance in the design (Refer Slide Time: 15:02). So, that is this, integration will occur in this frequency region, the integrator is not used

below the frequencies f_c . About the applications **applications** of the integrator, these are used in analog computation **analog computation** and in wave shaping circuits and of course, they are similar other uses. So, this was about the integrator or integrating amplifier using **(())**.

(Refer Slide Time: 16:17)

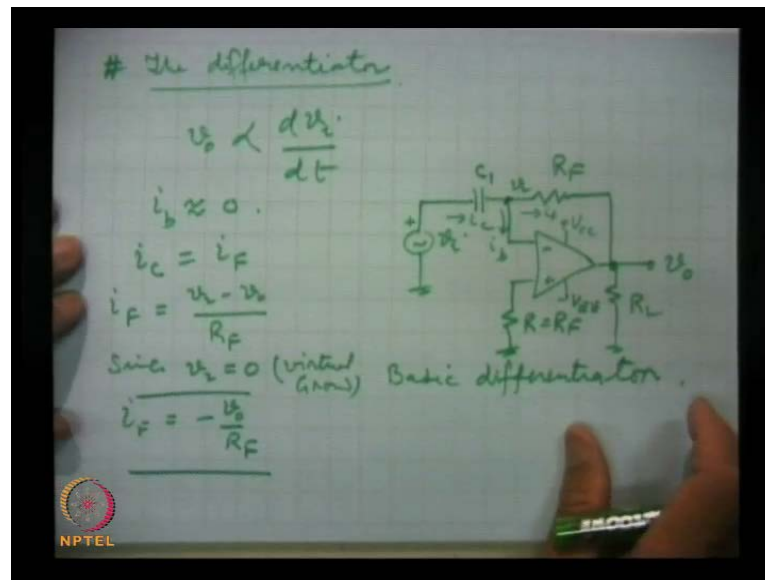

Next, we take a differentiator that is the, next in which we are considering the differentiator. In differentiator circuit, the output is proportional to the rate of change of the input at that instant. I repeat that, output in the differentiator is proportional to the rate of change of the input. And rate of change is as we will see; that means, what I am saying is this, is proportional to when input signal is v_i and output is proportional to this and this is this circuit is called **differentiating** differentiator or differentiating amplifier.

And this can be again realized in inverting amplifier. Inverting amplifier, **the capacitor R** **1** the **the** resistor R_1 is replaced by the capacitance, then the circuit works as a differentiator. So, if the resistance R_1 of inverting amplifier is replaced by the capacitance capacitor, then this is the circuit (Refer Slide Time: 17:48), (No audio from 17:49 to 17:59) this is R_f , this is C_1 and here this is v_i , the resistance which is equal to roughly R_f and here, is the load resistor across which we take the output, this is the basic differentiator, basic.


And of course, this power supplies are there, which are not essential to be shown, because it is implied that, they are **they are** no electronic repeatedly I am saying, no

electronic circuit will function, unless the transistors of this in the device are properly biased and for biasing we need the d c supply. So, **this is** these are two supplies here.

This is the charging current i_c , which the signal will send v_i will send and here is current i_f , this is i_f , this is the small current i_b ; and i_b this repeatedly is being said that, i_b because, the input impedance is very high of the device it is in 1 or 2 **(())**. So, i_b can be taken as 0, if i_b is taken 0; that means, no current is going in this arm, in the inverting input then, we can write i_c equal to i_f **i_c equal to i_f** .

And how much is i_f , i_f this current two voltages, this is v_2 this is v_0 . So, v_2 minus v_0 by R_F this is this. But we know that, v_2 the inverting input is at virtual ground potential, so since v_2 is 0 virtual ground everywhere we are seeing, the advantages in inverting amplifier, the advantages of virtual ground, because the concept of virtual ground makes the analysis much simpler. So, this is virtual ground. Then i_f is equal to minus v_0 by R_F , this is one expression (Refer Slide Time: 21:23).

(Refer Slide Time: 21:44)

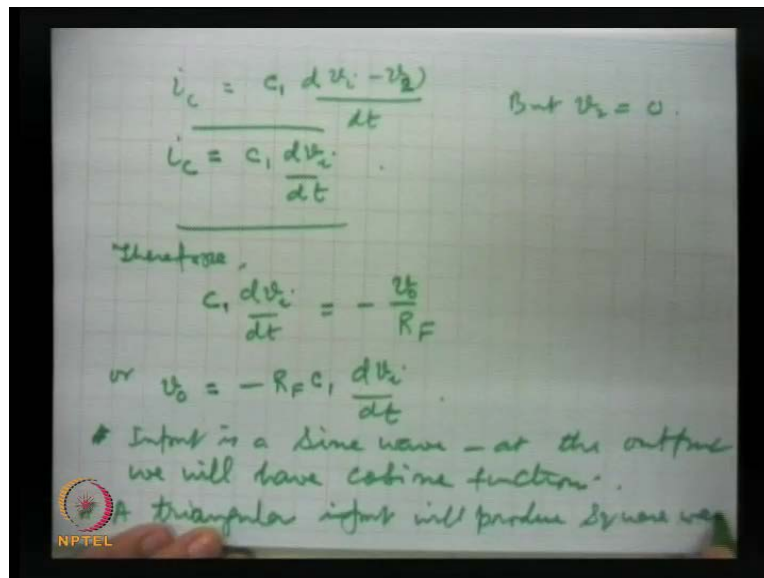


And how much is i_c ? The charging current **charging current** we can write i_c , this is equal to the capacitance into, from simple capacitors theory and voltage difference, so v_i minus v_0 by $d t$ and **sorry** the two voltages, this is at v_i and this is at v_2 . So, this is 2 (Refer Slide Time: 22:10), v_2 which is 0. But, v_2 is 0 and hence i_c equal to $c_1 d v_i / d t$ hence, because the two currents are identical here, i_c is equal to i_f .

So, these two expressions we **we** have already got for i_f and here this is for i_c and so, we can write therefore, **therefore** $c \frac{d v_i}{d t}$, this is equal to $\frac{v_0}{R F}$ or v_0 is equal to $\frac{v_0}{R F} c \frac{d v_i}{d t}$. This is what we said in the beginning that, this is all constant and this sine inversion is does not make a difference this also we have been talking and so, the output is proportional to the rate of change of input.

So, let us take two cases, when input is a sine wave, **input is a sine wave** output will appear as cosine, at the output we will have cosine function cosine wave. And for triangular input, a triangular **triangular** input will produce a square wave output **will produce square wave output**. Now, we talk about again, because for these integrators and differentiators, frequency response is very important. When the input frequency thus, the frequency of the input signal is changing then, how the output will vary that is of significance.


(Refer Slide Time: 25:35)

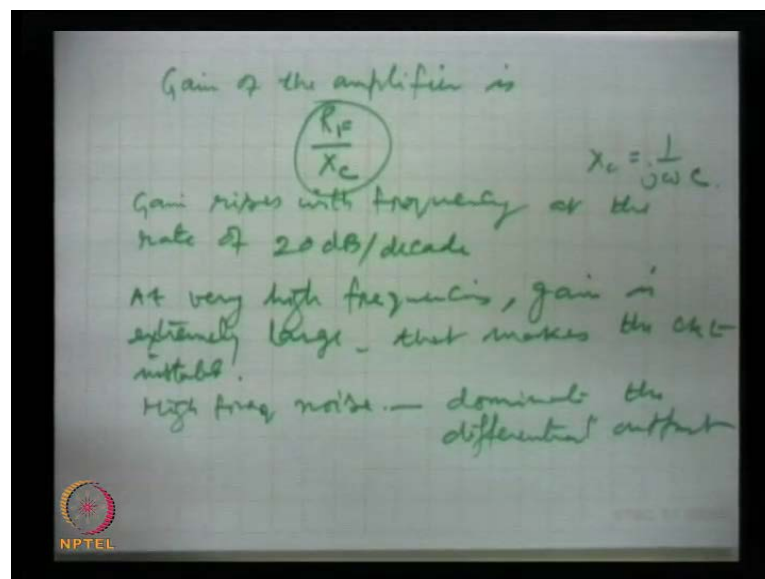

Now here, we **we** should note in this basic circuit of differentiator. There are two problems, one is that gain of the amplifier **gain of the amplifier** is $R F$ by $X c$, where $X c$ is the this is you know for the inverting amplifier, the gain used to be $R F$ by $R 1$, $R 1$ was the resistance here (Refer Slide Time: 26:07). Now, here it is the capacitance. So, the resistance will be replaced by the reactance; and this reactance will go low very fast with at higher frequency, because this is $X c$ is $\frac{1}{j \omega c}$.

So, at low frequencies this is at high frequencies, this is very low and therefore, gain rises with frequency **with frequency** at the rate of **at the rate of** 20 dB per decade of frequency; that means, when frequency becomes ten times, then it changes ten times, so 20 dB. So, this is the change, and at very high frequencies, this will be very low and gain will become very large. At very high frequencies, gain is extremely large and that makes the circuit **(()) that makes the circuit (())** and that way, the frequencies noise they will also may get amplified. Now because of this, there is a high frequency noise which will be heavily amplified, and that will dominate the differential output **differential output**. So, **it will** it will not be an accurate differentiation at very high frequencies.

(Refer Slide Time: 29:29)

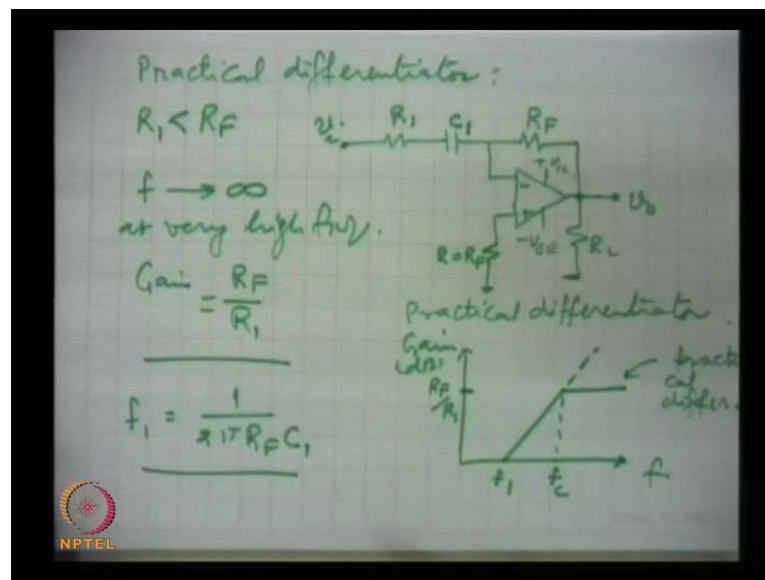

So, to take care of this fact, that gain becomes exceedingly high, when the frequencies are very high. We attach a small value resistor and we get a practical differentiator **practical differentiator** is this (Refer Slide Time: 29:37), (No audio from 29:38 to 29:54) this is R_F , this is the resistance R_1 which we have attached, and R_1 is quite a smaller as compared to R_F ; and this is C_1 and here, we attach the input signal, this resistance is equal to R_F and these are the supplies. This is the practical differentiator **practical differentiator**.


And here, now at very low frequencies frequency of the signal tending towards infinity at very high frequencies **at very high frequencies**. Here (Refer Slide Time: 31:09), the gain was rising very fast with the fall in X_c at in this case, now when this is almost is a short,

then gain will be restricted to this. And this normally may be 10, 12, 15, so gain will be this at very high frequencies; and the frequency response of this practical differentiator is this and here, this was the gain going up very fast with frequency, this is frequency (Refer Slide Time: 31:54), and this is in d B.

Now here, for the practical one, the gain will state very high frequencies when this capacitor is almost acts as a short at those frequencies, the gain will be this here; this is R_F by R_1 . So, this is the response of a practical differentiator, this is practical differentiator, this was for the ideal one, this is for the **the** basic which we have showed the integrator, basic integrator and this is the practical integrator.

And here (Refer Slide Time: 32:51), this frequency is f_2 or f_c we can say and this is f_1 , f_1 is the frequency, where the gain will fall to 0. And f_1 will be given by, f_1 is 1 by $2\pi R_F C_1$ at the frequency at which this becomes a the gain becomes 0. So, this is the frequency.

(Refer Slide Time: 33:58)

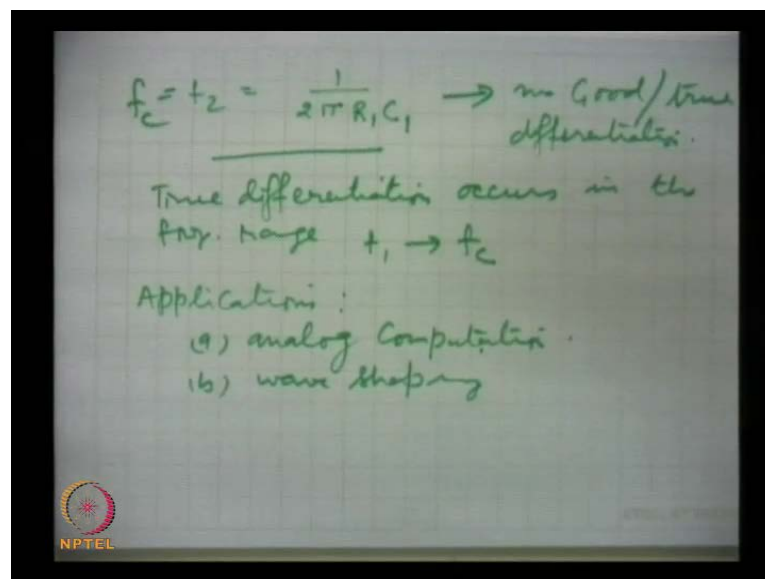


And the inclusion of R_1 that has restricted that limits the high frequency range of the differentiator, and this f_c will be given by, f_c is given by $2\pi R_1 C_1$. So, again as in differentiator we have two frequencies, f_2 which is same as f_c which I have written here, this we can write f_2 or f_c , this is this frequency (Refer Slide Time: 34:09), and this is the **the** difference is of R_1 and R_F . So, beyond this frequency f_2 , no **no** good differentiation, no true differentiation of the input will appear.

And so, differentiation is there in the frequency, true differentiation occurs in the frequency range f_1 to f_c or f_2 whatever you write. And this frequency is set f_c is set quite high in comparison to f_1 , so that there is a good range of frequencies over which true differentiation will be possible about applications, this is we have discussed.

So, the basic circuit is not used for differentiator, but this circuit is used by inclusion of resistance R_1 and this is the frequency response of the practical differentiator, the inclusion of R_1 puts a limit on the high frequency; that means, a safes the circuit from (()) of very high gain; and so, a true differentiation occurs between the range f_1 and f_c .

And about the applications of differentiator, they are the same as the integrator that, they are used in analog analog computation and wave shaping. So, this is all about the differentiator. So, we have taken several applications, we continue with few more and that will show the versatility of the operation amplifier. So, after these summing circuits and differentiator, integrators, sine changer and we now go for another class of of applications, and these are active filters.

(Refer Slide Time: 37:18)

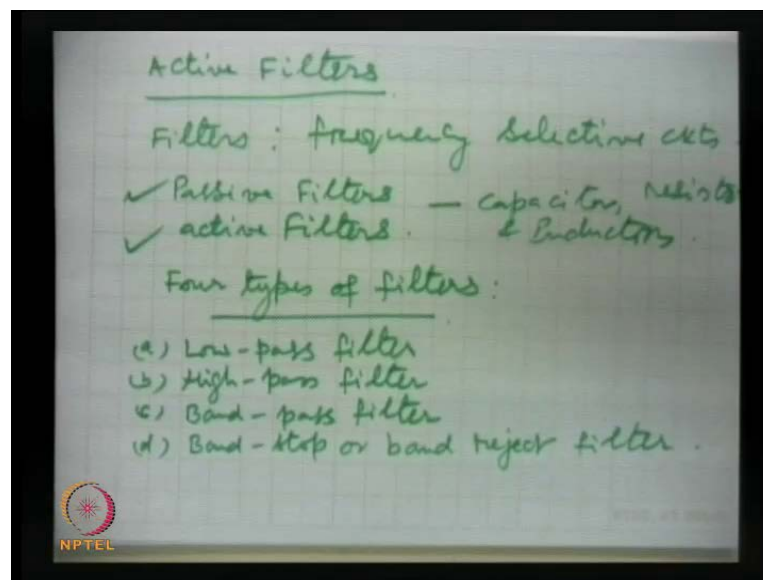

Active filters first thing is, what is a filter? Filter is a frequency selective circuit. Frequency selective; that means, you have a spectrum of frequencies and you want to select for your system that your system should respond to certain frequencies. So, how to get them? Frequency selection can be done in by using filters, filter circuits.


Now, there are two types of filters, passive filters and active filters. Filters, these are frequency selective circuits, and they can be two types, passive filters and active filters **passive filters and active filters**. Now, passive filters can be realized frequency selection circuits you can make by using capacitors, resistors and inductors, you must have done, you have done a resonance circuit.

What is a resonance circuit? Resonance circuit is a frequency selective circuit, and resonance can be obtained by the combination of capacitor, resistance and inductors. But, these filters the passive, these are called passive filters, they are inefficient; inefficient in the sense, there are two points, one is that these components will dissipate certain signal. So, signal is attenuated in passive filters number 1. Second thing is that frequency response of passive filters is not as good as in the case of active filters.

So, active filters are the ones, which make use of the active device, transistors or **(())** to make filters, operational amplifiers are very widely used in fact, they have replaced B J T and all other circuits, for making active filters; because, handling of operation amplifiers is not at all difficult plus, they are not expensive. And hence, active filters make use of operation amplifiers and these circuits are very widely used.

Now, there are four types of filters, four types, four types of filters. What are these types? First I name them and then, I will elaborate them. One is low pass filter **low pass filter** then, we have high pass filter, we have band pass filter and then finally, we have band stop **band stop** or band reject filter **or band reject filter**. These are the four different kinds of filters, depending on the selection of frequencies for the working of the circuit at which frequencies we want to choose. And in signal processing, this filtering of frequencies is a very important process and so, we now first talk about these filters.

(Refer Slide Time: 43:00)

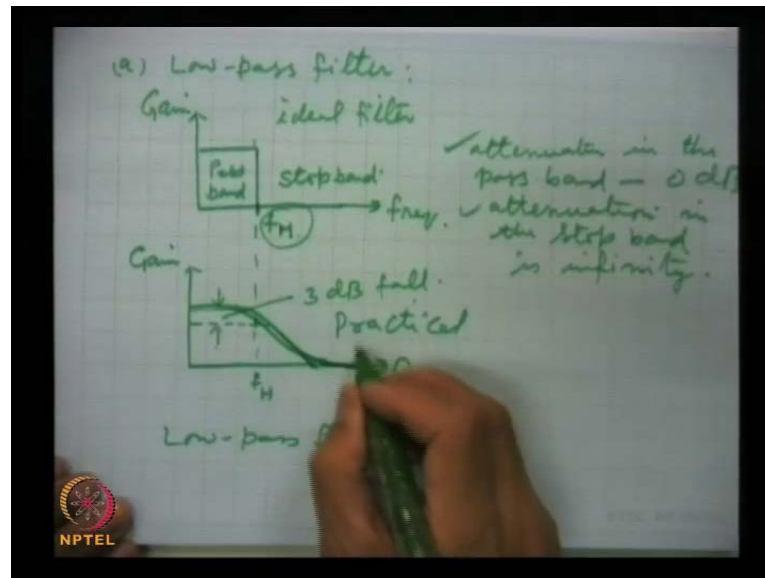

The low pass filter, first we take low pass filter. Low pass filter is the one, which is supposed to pass, by pass we mean that they will go in the circuit for further processing. So, certain frequencies from very low to a certain high frequency, they will be allowed to propagate beyond that frequency signals will attenuate **heavily** very heavily and they will be prohibited from going for further processing, so that will be low pass filter.

The ideal first I take ideal low pass filter, then the actual low pass filter practical. So, this is the case, this is gain and this is frequency, this is the pass band, this is frequency, so this is pass band (Refer Slide Time: 44:17), and all these is stop band and let us, call this frequency as f_H and this is ideal.

So, what is the low pass filter, from 0 frequency to upto a maximum of say f_H frequency, it will pass; that means, signal will pass through the circuit without attenuation and **it will be** it has been selected in this frequency range it will be selected and it will be further processed. And in ideal, this is the case of ideal filter, in which gain the attenuation in the pass band **attenuation in the pass band** in the ideal filter is 0 dB that means no attenuation; while attenuation in the stop band, stop band is infinity infinitely high attenuation. So, this is for ideal filter.


Now, electronically we cannot have this ideal gain frequency response, because there is no process by which this break can be that sharp. So, the practically what we have is this (Refer Slide Time: 46:25), (No audio from 46:26 to 46:39) here (No audio from 46:42 to

46:51) we have this frequency is f_H . And so here, this gain this is 3 d B fall **3 d B fall** and this is frequency (Refer Slide Time: 47:19).

So, this is the case that gain will start falling here and then, it will go and fall very fast here and upto this frequency 3 d B fall will be corresponding very close to f_H here (Refer Slide Time: 47:36). The **the** fall will start and 3 d B has falling by this frequency, cut off frequency and beyond that, again in the ideal case, it was infinite attenuation here, that at loss the attenuation will be high, but it continues for certain frequency region.

So, this is the response and we will drive an expression for this cut off. What is the highest cut off, for the low pass filter? In this, we can design we can choose it can be 5 kilo hertz; it can be 50 kilo hertz depending on our requirement. So, this is the case of low pass filter, this is the practical filter, this is practical case practical filter.

(Refer Slide Time: 48:55)

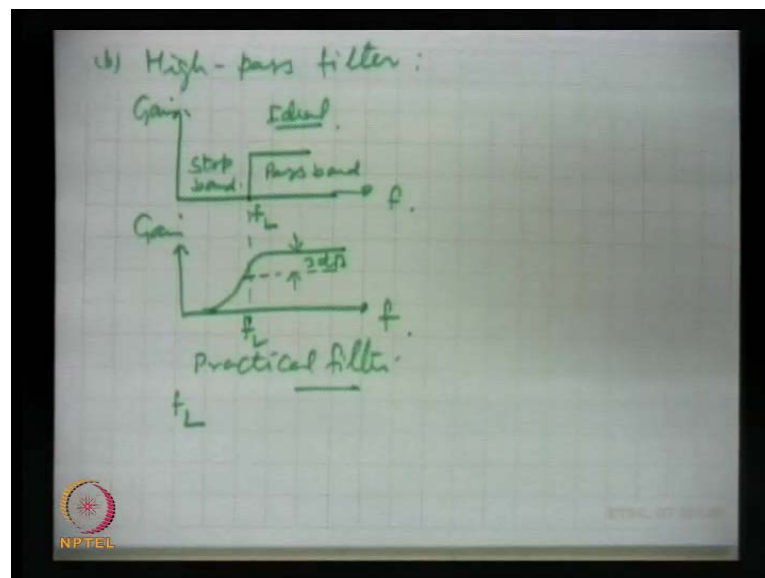


Then we go for high pass filter **high pass high pass filter** the ideal case is here, this is pass band (Refer Slide Time: 49:06), and this is stop band, this is gain and here, this is of course, frequency. So, this is the ideal **ideal** filter, where the attenuation in the stop band is infinity; and from this frequency, which is the lowest frequency from where the pass band start, the attenuation is 0. But, this 0 and infinity again, these are ideal and this sharp boundary between stop band and pass band, this is also only ideal.

In the practical case, this circuit this response for the **the** actual filter will be like this (Refer Slide Time: 50:12), this is gain and this gain is 3 d B, and this frequency will be f_L say, this is frequency. So, this is the response of the high pass filter, this is the practical. And we will arrive at an expression for this f_L that is lowest frequency in this we can choose as I said, depending on the circuit components.

Now, the active filters as I said, will make use of **(C)** capacitors and resistors, just few capacitors and resistors and filter design will be complete, the inductors are not used; there are reasons, and these reasons are inductors are bulky and heavy, and they are not **(C)** and hence, inductors are not used with active filters. So, this is the case of high pass filter.

(Refer Slide Time: 51:48)

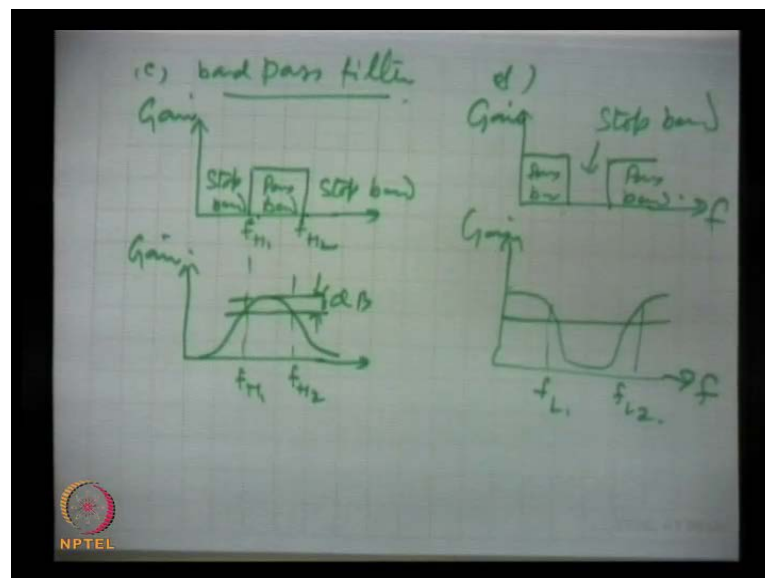

And then, we can have the band pass filter, c band pass filter. The band of frequencies is allowed before that, they it is not permitted, after that it is not permitted; and for the ideal, this is the case (Refer Slide Time: 52:04), this is gain and this is pass band, this is stop band, this is also stop band. But practically, these are the frequencies f_{H1} and f_{H2} ; that means, **for this** these frequencies line between the pass band, the attenuation will be very low; very heavy in the smaller frequency region and very heavy in the higher frequency region.

And for the practical one, this plot is like that (Refer Slide Time: 52:44), and here this is 3 dB change again, 3 dB and this is f_{H1} , f_{H2} gain. So, this is the **the** band pass, band of frequencies will pass, rest will be stopped.

And finally, we have the last one, the band reject or band stop. This is ideally it is this (Refer Slide Time: 53:27), this is pass band, this is pass band, this is the stop band, this is gain, this is frequency and this is that. And practically this will be like this (Refer Slide Time: 53:50), where this is gain, this is frequency, and these are those two frequencies, f_{L1} , f_{L2} . So, this band will not be permitted to go in the circuit for further processing. So now, we will go one by one about these in details, the circuits and their analysis.